

COMPUTER INTERFACING TO AN NTC THERMISTOR



Using a precision NTC thermistor as a sensor for a uC or computer based instrument can be accomplished in a fairly straightforward manner. A thermistor/resistor voltage divider bridge can supply a strong signal to an A-D converter, which can then be interfaced to the desired instrument (Figure 1). Using the entire range of the thermistor (-55°C to 125°C), a 12 bit A-D can give a resolution of 0.04°C, a 10 bit 0.175°C and an 8 bit 0.70°C. Since an NTC thermistor exhibits a nonlinear change in resistance with a linear change in temperature, the voltage output of the bridge must be interpreted for the actual temperature. This can be accomplished with an R-T look up table, or through the use of an equation which characterizes the thermistor response.

APPLICATION USING AN R-T LOOK UP TABLE

Using this method, the A-D count is simply used as an offset to correlate to the temperature recorded in the table. The table is created by calculating or measuring the A-D count when the thermistor is at a given temperature or resistance value, and recording this in the table. This method has the advantage of the ability to manipulate the table to fit a particular thermistor's R-T characteristic very closely.

The following example uses a 10K ohm thermistor/10K ohm fixed resistor bridge network, and an 8 bit A-D converter.

R-T multiplier @ -55°C = 96.4	Bridge voltage @ 125°C = 0.00048V
Thermistor R @ -55°C = 964K ohm	R-T multiplier @ 25°C = 1
Bridge voltage @ -55°C = 4.948V	Thermistor R @ 25°C = 10K ohm
R-T multiplier @ 125°C = .03461	Bridge voltage @ 25°C = 2.5V
Thermistor R @ 125°C = 346.1 ohm	

Using these values, the A-D high ref would be set at 4.984V, and the low ref at 0.00048V, yielding (4.984V-0.00048V)/256 count or ~0.0194V per A-D count, giving the following:

A-D count at 125°C = 00000000, table element 0 = 125
 A-D count at -55°C = 11111111, table element 255 = -55
 A-D count at 25°C = 2.5V/0.0194V = 128.8dec = 10000001bin, table element 129 = 25

The in-between values are calculated in the same manner. The number of values in the table can be any power of 2 up to the resolution of the A-D converter. By dividing the A-D count by the appropriate number and using linear interpolation between the table entry numbers, required table memory space can be reduced with a minimum decrease in accuracy.

```

DIM TABLE (255) AS SINGLE 'this is the lookup table
TABLE (0) = 125
.
.
.
TABLE (129) = 25
.
.
.
TABLE (255) = -55
OPEN "A-D" FOR INPUT AS #1 'open A-D
INPUT #1, ADCOUNT 'and get count
TEMP = TABLE (ADCOUNT) 'get temperature at pointer
PRINT TEMP 'and the final output in degrees Celsius
  
```

The following is an example in BASIC how to implement this using a 64 element lookup table and 8 bit A-D converter.

```

DIM TABLE (64) AS SINGLE          'this is the lookup table
  TABLE (0) = 125
  .
  .
  TABLE (32) = 25                 'this is ~129/4
  .
  .
  TABLE (63) = -55
  .
  .

OPEN "A-D" FOR INPUT AS #1        'open A-D
INPUT #1, ADCOUNT                 'and get count
TABLEOFFSET = INT(ADCOUNT/4)      'divide by 4 for lookup table of 64 elements. Round result to next lowest
                                  integer value.

TEMP = TABLE (TABLEOFFSET)       'get temperature at pointer
NEXTTEMP = TABLE (TABLEOFFSET+1) 'get temperature above pointer (next 'pointer location). Actual temperature
                                  is between these two.

DIFFTEMP = ABS (ADCOUNT-(TEMP*4)) 'this is the distance from TEMP between TEMP and NEXTTEMP. This is the
                                  interpolated temperature. Remember that values in table decrease as the
                                  A-D count increases. Note that this assumes that a table point lies on 0. If
                                  there is no 0 entry separating positive and negative table entries, some
                                  additional conditions must be added to correctly interpolate.

INTERPTEMP = TEMP +
  (((TEMP-NEXTTEMP)/4)*DIFFTEMP)
PRINT INTERPTEMP                  'and the final output in degrees Celsius.

```

APPLICATION USING THERMISTOR CHARACTERIZATION EQUATION

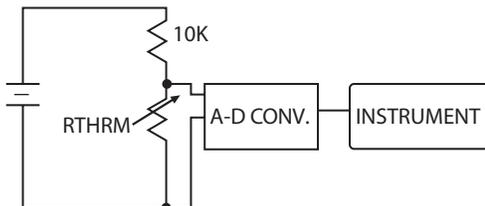


Figure 1. (Left) A thermistor/resistor voltage divider bridge can supply a strong signal to an A-D converter, which can then be interfaced to the desired instrument.

```

a = ?                             'these constants need to be entered
b = ?
c = ?
d = ?

resolution = 256                  'for 8 bit A-D
vref = 5                          'bridge voltage
rfix = 10000                      'fixed bridge resistor

OPEN "A-D" FOR INPUT AS #1        'open A-D
INPUT #1, ADCOUNT                 'and get count
VBRIDGE = ADCOUNT*(vref/resolution) 'convert to voltage across thermistor
R THERM = VBRIDGE/((vref-VBRIDGE)/rfix) 'find thermistor resistance. Convert to temperature using given
                                       coefficients and equation. This is the standard Steinhart-Hart
                                       equation, with the 273.15 added to yield degrees Celsius.

TEMP = (1/(a + b*(LnR THERM) + c*(LnR THERM)^2 +
  d*(LnR THERM)^3)) - 273.15
PRINT TEMP                        'and the final output in deg C

```

ABOUT CTS CORPORATION

Founded in 1896, CTS Corporation (NYSE: CTS) is a leading designer and manufacturer of products that Sense, Connect, and Move. The company manufactures sensors, actuators, and electronic components in North America, Europe, and Asia. CTS provides solutions to OEMs in the aerospace, communications, defense, industrial, information technology, medical, and transportation markets. CTS focuses on providing advanced technology, exceptional customer service and superior value to industry partners throughout the globe.

CTS aims to be at the forefront of technology, delivering innovative sensing, connectivity and motion solutions for the creation and advancement of products and services around the world.

LEARN MORE

If you would like to learn more about how CTS can help you, please contact us today. We would be happy to discuss your project with you and help with the product selection process. Additionally, if you are unable to find the item you need, our engineers may be able to produce a custom component for your individual application.